

Tutorial 9: Solution

NB It is possible to solve these problems in more than one way. These are typical solutions.

Problem 1: INC(Increment) Result = Number + 1

State 1: Load the instruction register

State 2: Clear Register A by setting zero on the ALU

State 3: Load the number into B

State 4: Load the Instruction register

State 5: Add A and B with the carry in set to 1, shifter unchanged, load the result into RES

State	Data In	Instruction register (IR)							
		IR7	IR6	IR5	IR4	IR3	IR2	IR1	IR0
1	0000000X	X	X	X	X	X	X	X	X
2	XXXXXXXXXX	0	0	0	0	0	0	0	X
3	Number	0	0	0	0	0	0	0	X
4	X0110000	0	0	0	0	0	0	0	X
5	XXXXXXXXXX	X	0	1	1	0	0	0	0

Problem 2. FN1(A+B-C)/2 Result = (Number1+Number2-Number3)/2

State 1: Load the instruction register

State 2: Load Number 1 into A

State 3: Load Number 2 into B

State 4: Load the instruction register

State 5: Clear C by setting the ALU to zero

State 1: Load the instruction register

State 2: Add A and B with zero carry in, Load the result into A

State 3: Load Number 3 into B (assume that there is no carry from the previous stage)


State 4: Load the instruction register

State 5: Subtract B from A, set the shifter to shift right, load result into RES

State	Data In	Instruction register (IR)							
		IR7	IR6	IR5	IR4	IR3	IR2	IR1	IR0
1	1XXXXXXXXX	X	X	X	X	X	X	X	X
2	Number 1	1	X	X	X	X	X	X	X
3	Number 2	1	X	X	X	X	X	X	X
4	X000XXXXX	1	X	X	X	X	X	X	X
5	XXXXXXXXXX	X	0	0	0	X	X	X	X
1	00110001	X	0	0	0	X	X	X	X
2	XXXXXXXXXX	0	0	1	1	0	0	0	1
3	Number 3	0	0	1	1	0	0	0	1
4	X0101101	0	0	1	1	0	0	0	1
5	XXXXXXXXXX	X	0	1	0	1	1	0	1

Problem 3

Both multiplexers could be set from IR7.

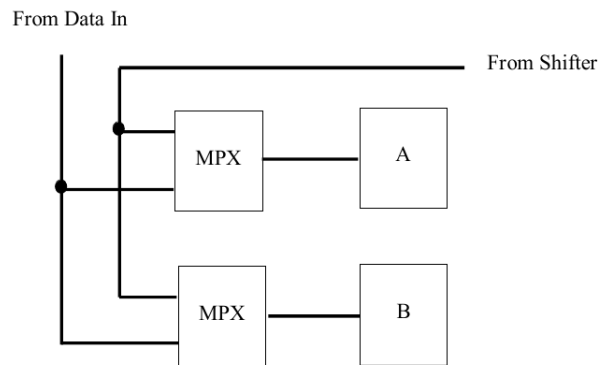

Alternatively we could use the basic shifter which has just four functions and therefore two function select bits, and use the spare bit to set the multiplexer on the input to B.

Another possibility is to decode the IR. Using the bits directly is very inefficient. We will explore this idea in more detail in the last lectures of the course.