

Computer Systems - Architecture

Lecture 4 - Boolean Logic

Eddie Edwards
eedwards@doc.ic.ac.uk

<http://www.doc.ic.ac.uk/~eedwards/compsys>
 (Heavily based on notes by Andrew Davison and
 Ian Harries)

Computer Systems - Architecture (EEwards)

Boolean Logic (4.1)

Learning Outcomes

- At the end of this lecture you should:
 - understand how logic relates to computing problems
 - be able to represent Boolean logic problems as:
 - Truth tables
 - Logic circuits
 - Boolean algebra
 - be able to produce circuits for the half adder and full adder
 - have a feeling for how electronic circuits can be joined together to create number manipulators (simple computers???)

Computer Systems - Architecture (EEwards)

Boolean Logic (4.2)

What is Logic?


- Dictionary definitions (dictionary.com - reduced!)
 - reason or sound judgement
 - a system of principles of reasoning
 - the science that investigates the principles governing correct or reliable inference
- Branch of philosophy
 - Principles of inference
 - Ancient civilizations (India – the Rigveda, China Gongsun Long – 325 BC)
 - Greek – Aristotle (Syllogistic logic)
 - Modern: John Stuart Mill "The science of reasoning", Frege, Russell, Gödel...
- You use logic all the time in your everyday life

Computer Systems - Architecture (EEwards)

Boolean Logic (4.3)

Boolean Logic

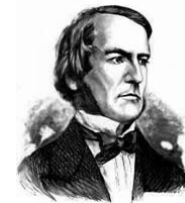- Named after George Boole
- Provides a system of logical operations
- Rules for combining operations
- Describes their application to binary numbers



0 or 1?
TRUE or FALSE?
YES OR NO?

Computer Systems - Architecture (EEwards)

Boolean Logic (4.4)

Simple Example

- "If it is raining then I will take an umbrella"
 - "It is raining" – can be TRUE or FALSE
 - "I will take an umbrella" - can be TRUE OR FALSE
- The truth of "take an umbrella" *depends on* the truth of "raining"
- Can be represented in the form of a truth table:

Raining	Umbrella
False	False
True	True

Can be used to make a decision (i.e. inference):
 (take umbrella) = (raining)

Computer Systems - Architecture (EEdwards)

Boolean Logic (4.5)

Example 2

"If it is raining or the weather forecast is bad then I take an umbrella"

Truth table:

Raining	Bad forecast	umbrella
False	False	False
False	True	True
True	False	True
True	True	True

(take umbrella) = ((raining) OR (bad forecast))

Computer Systems - Architecture (EEdwards)

Boolean Logic (4.6)

Example 3

"If it is raining and I have no car then I will take an umbrella"

Truth table:

Raining	No Car	Umbrella
False	False	False
False	True	False
True	False	False
True	True	True

(take umbrella) = ((raining) AND (NOT car))

Computer Systems - Architecture (EEdwards)

Boolean Logic (4.7)

Digital Logic

- Computers make decisions using logic
- Basic logic operations
 - NOT
 - AND
 - OR
 - Exclusive OR (XOR)
- Also
 - NOT AND (NAND)
 - NOT OR (NOR)

Computer Systems - Architecture (EEdwards)

Boolean Logic (4.8)

Digital Logic


- Computers operate electronically using **Logic Gates**
 - One or more inputs
 - One output
 - Input and output are binary digits (0 or 1)
 - 0 = FALSE
 - 1 = TRUE
- Electronic circuits are easily connected together to perform more complex functions, from these basic “building blocks” of computers

Computer Systems - Architecture (EEwards)

Boolean Logic (4.9)


Logic Gates

NOT gate:

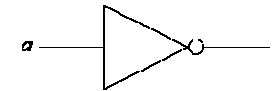

a	x
0	1
1	0

AND gate:

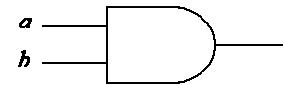

a	b	x
0	0	0
0	1	0
1	0	0
1	1	1

Computer Systems - Architecture (EEwards)

Boolean Logic (4.10)

What is the truth table for the NOR gate?

a	b	x
0	0	1
0	1	1
1	0	1
1	1	0

A

a	b	x
0	0	1
0	1	0
1	0	0
1	1	0

B

a	b	x
0	0	0
0	1	1
1	0	1
1	1	0

C

a	b	x
0	0	0
0	1	1
1	0	1
1	1	1

D

a	b	x
0	0	0
0	1	0
1	0	1
1	1	1

E

Computer Systems - Architecture (EEwards)

Boolean Logic (4.11)


Logic Gates

OR gate:



a	b	x
0	0	0
0	1	1
1	0	1
1	1	1

XOR gate:

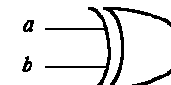

a	b	x
0	0	0
0	1	1
1	0	1
1	1	0

Computer Systems - Architecture (EEwards)

Boolean Logic (4.12)

How many basic logic gates are required

- NOT
- AND
- OR
- XOR – can be made up of NOT, AND and OR gates
- Draw the circuit.....

- What is the corresponding logic equation?

Computer Systems - Architecture (EEwards)

Boolean Logic (4.13)

Answer

- A $a \text{ (XOR) } b = (\text{NOT } a) \text{ AND } (\text{NOT } b) \text{ OR } (a \text{ OR } b)$
- B $a \text{ (XOR) } b = a \text{ OR } ((b \text{ AND NOT } a) \text{ AND } b)$
- C $a \text{ (XOR) } b = \text{NOT}((\text{NOT } a \text{ AND NOT } b) \text{ OR } (a \text{ AND } b))$
- D $a \text{ (XOR) } b = (a \text{ AND NOT } b) \text{ OR } (\text{NOT } a \text{ AND } b)$
- E $a \text{ (XOR) } b = (a \text{ OR } b) \text{ AND NOT } (a \text{ AND } b)$


IN FACT C, D or E are correct answers, but D,E more concise

Computer Systems - Architecture (EEwards)


Boolean Logic (4.14)

Summary

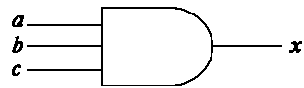- Basic logic gates AND, OR and NOT are enough
- Useful to have others - XOR, NAND etc.
- Can have more complex gates (e.g, multiple inputs)



3-input AND gate


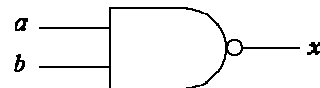


NAND gate
(AND followed by NOT)

Computer Systems - Architecture (EEwards)

Boolean Logic (4.15)

Practical digital circuits

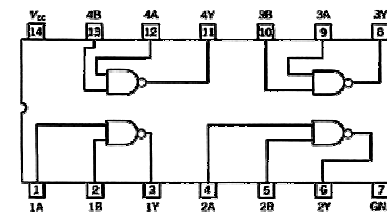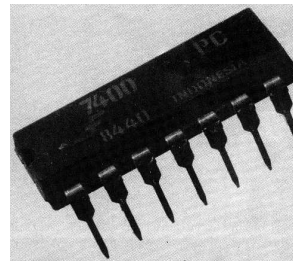

7400 dual in-line package

Computer Systems - Architecture (EEwards)

Boolean Logic (4.16)

Boolean algebra - notation

Infuriatingly, there is no single agreed representation for the logical operators in Boolean algebra:

$$\mathbf{A \text{ AND } B} \circledR \mathbf{A \cdot B} \circledR \mathbf{A \dot{\cup} B} \circledR \mathbf{A \& B} \circledR \mathbf{AB}$$

$$\mathbf{A \text{ OR } B} \circledR \mathbf{A + B} \circledR \mathbf{A \dot{\cup} B} \circledR \mathbf{A | B}$$

$$\mathbf{A \text{ XOR } B} \circledR \mathbf{A \dot{\Delta} B}$$

$$\mathbf{NOT A} \circledR \mathbf{A \complement} \circledR \mathbf{\emptyset A} \circledR \mathbf{\bar{A}} \text{ (with bar)} \circledR \mathbf{A'}$$

We will use $A \cdot B$, $A + B$, A'

Computer Systems - Architecture (EEEdwards)

Boolean Logic (4.17)

Boolean algebra - rules

There are many rules that can be used for algebraic manipulation

Negation:

$$(A')' = A$$

$$A \cdot A' = 0$$

$$A + A' = 1$$

Associative:

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A + B) + C = A + (B + C)$$

Commutative:

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

Distributive:

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

Note the precedence

Computer Systems - Architecture (EEEdwards)

Boolean Logic (4.18)

Boolean algebra - rules

Single variables:

$$A \cdot A = A$$

$$A + A = A$$

Simplification rules with 1 and 0:

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

Computer Systems - Architecture (EEEdwards)

Boolean Logic (4.19)

Boolean Algebra – de Morgan's rules

$$(A + B)' = A' \cdot B'$$

$$(A \cdot B)' = A' + B'$$

as before, A and B can be any Boolean expression

Can generalise to n Boolean variables:

$$(A + B + C + D + \dots)' = A' \cdot B' \cdot C' \cdot D' \cdot \dots$$

$$(A \cdot B \cdot C \cdot D \cdot \dots)' = A' + B' + C' + D' + \dots$$

Computer Systems - Architecture (EEEdwards)

Boolean Logic (4.20)

Boolean algebra – rules for XOR

$$A \oplus B = A \cdot B' + A' \cdot B$$

Complement Law for XOR:

$$(A \oplus B)' = A \oplus B' = A' \oplus B$$


Exclusive NOR (NOT XOR) sometimes called an equivalence gate – why?

Addition using logic gates

- Suppose we want to add two one-bit inputs?
- What is the truth table for
 - The sum?
 - Any bit that might carry over?

Addition using logic circuits

In the following circuit:

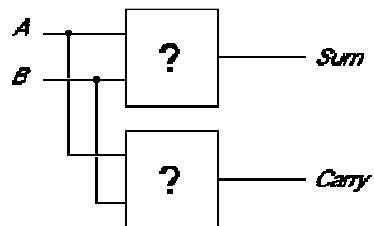

Upper box is: A. AND B. OR C. NOT D. XOR E. NOR

Lower box is: A. AND B. OR C. NOT D. XOR E. NOR

The half-adder


The full adder

- For a full adder, we need another input, the carry bit from the next less significant bit.
- What is the logic circuit for the full adder?

Computer Systems - Architecture (EEwards)

Boolean Logic (4.25)


The full-adder

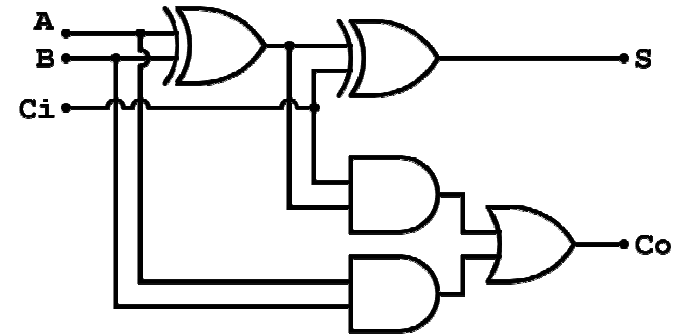

Computer Systems - Architecture (EEwards)

Boolean Logic (4.26)

The full adder - redrawn

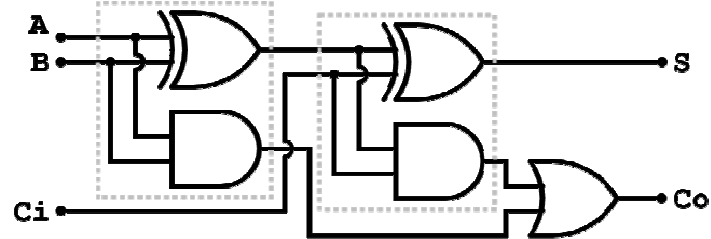

Effectively two half-adders plus an OR gate

Computer Systems - Architecture (EEwards)

Boolean Logic (4.27)

Learning Outcomes

- You should now:
 - understand how logic relates to computing problems
 - be able to represent Boolean logic problems as:
 - Truth tables
 - Logic circuits
 - Boolean algebra
 - be able to produce circuits for the half adder and full adder
 - have a feeling for how electronic circuits can be joined together to create number manipulators (simple computers???)

Computer Systems - Architecture (EEwards)

Boolean Logic (4.28)

This lecture - feedback

■ The pace of the lecture was:

A. much too fast B. too fast C. about right D. too slow E. much too slow

■ The learning objectives were met:

A. Fully B. Mostly C. Partially D. Slightly E. Not at all